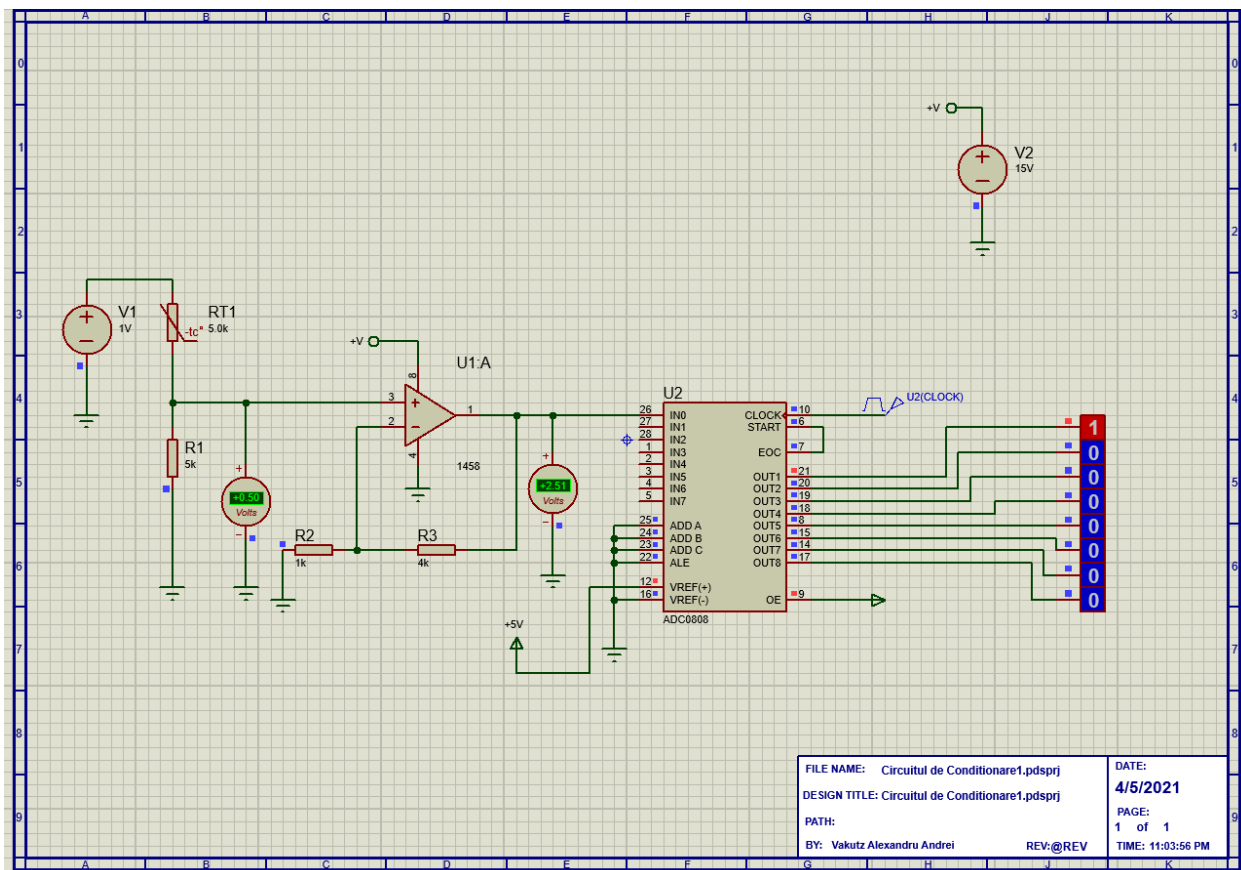


Project μ C – Part 3 – Conditioning Circuit

1.Introduction

To further process an analog signal, first it must be prepared. Here intervenes the conditioning circuit. In our case, it takes the output voltage of a voltage divider, amplifies it to fit in the 0-5V range, so that the ADC could read it and send it over to the μ C.

For the first sensor, which is an analog temperature sensor, I choose the temperature measurement range to be between 10°C and 45°C with a in between value, of 28°C.



2. Block Diagram



3. Components List

- Voltage sources x2
- Resistors x3
- NTC Thermistor x1
- 1458 Op Amp x1
- ADC 0808 x1

4. Calculus, circuit, and simulations

The chosen temperature sensor is the NI24MA0502H which has a R_T at 25°C of $5k\Omega$. To send data to the μC , it needs to be implemented in a voltage divider. Therefore, we require a second resistance, which I chose to be equal the R_T at 25°C :

$$R_1 = R_T@25 = 5k\Omega \quad (1)$$

$$V_{o1} = \frac{R_1}{R_1 + R_T} * V_{cc} \quad (2)$$

Where V_{o1} is the output voltage of the voltage divider and the V_{cc} is the input voltage which I chose to be 3.3V . Therefore, $V_{o1} = 1.65\text{V}$.

Since the ADC can intake a maximum of 5V I chose the A_v to be 1.51:

$$A_v = 1 + \frac{R_3}{R_2} = 1.51 \Rightarrow \frac{R_3}{R_2} = 0.51 \quad (3)$$

From equation 3 we can choose $R_3 = 51k\Omega$ and $R_2 = 100k\Omega$.

Now we can determine the ADC input:

$$V_{o2} = A_v * V_{o1} \quad (4)$$

Where V_{o2} is the output of the amplifier and the input to the ADC. Which will be:

$$V_{o2} = 2.49V$$

Now we can compute the value of the ADC:

$$ADC = \frac{V_{o2}}{V_{ref}} * 2^N \quad (5)$$

Where V_{ref} is 5V and N represents the number of output bits of the ADC.

$$ADC = 128 = 10000000_b$$

Which can also be verified by the following formula:

$$ADC = \frac{R_1}{R_1 + R_T} * 2^N \quad (6)$$

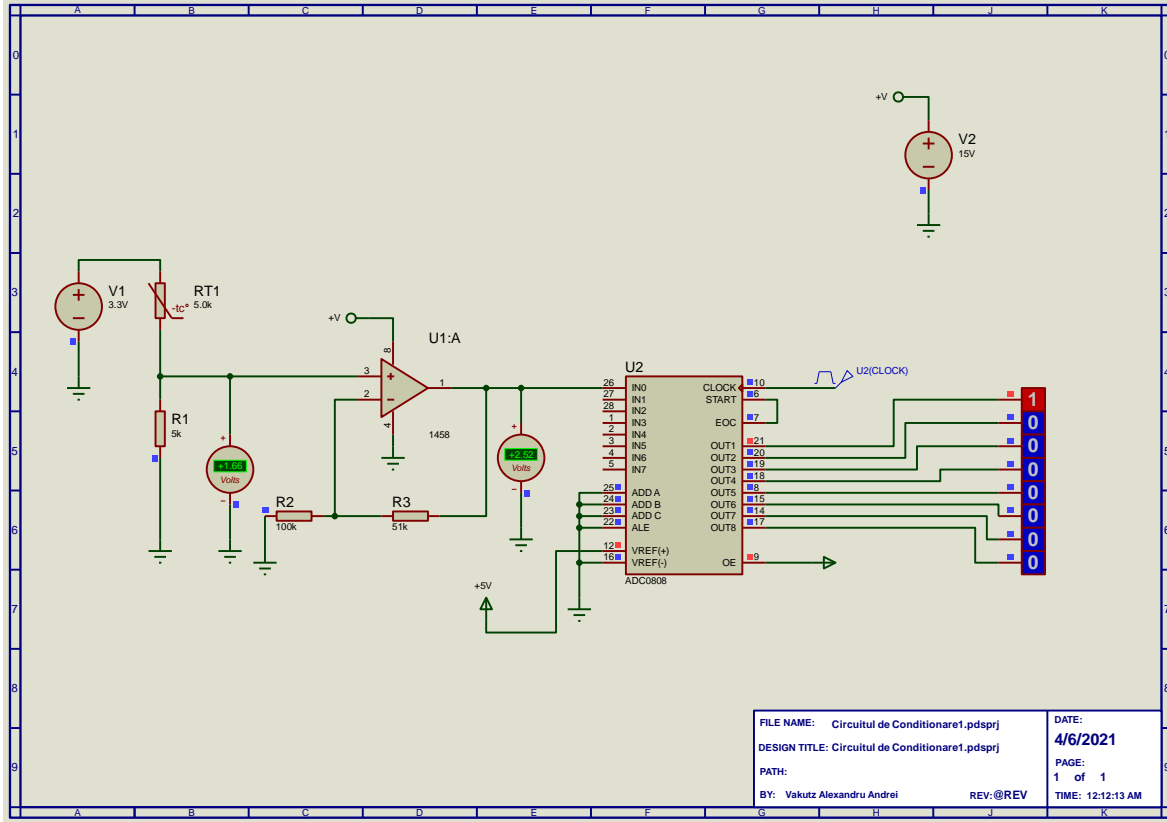


Figure 1. $R_T@25^\circ\text{C}$

For 45°C we will have $\text{ADC} = 1010\ 1111_b = 175$. With which we can determine the value of the thermistor (which is obtained by rearranging equation 6):

$$R_T = \left(\frac{2^N}{\text{ADC}} - 1 \right) * R_1 \quad (7)$$

In this case we will have: $R_T = 2.3\text{k}\Omega$

Following the same logic, we can determine the value of the thermistor at 10°C and at 28°C :

$$\text{ADC when } R_T@10^\circ\text{C} = 01100101 \Rightarrow R_T@10^\circ\text{C} = 12.65\text{k}\Omega$$

$$\text{ADC when } R_T@28^\circ\text{C} = 10001000 \Rightarrow R_T@28^\circ\text{C} = 9.4\text{k}\Omega$$

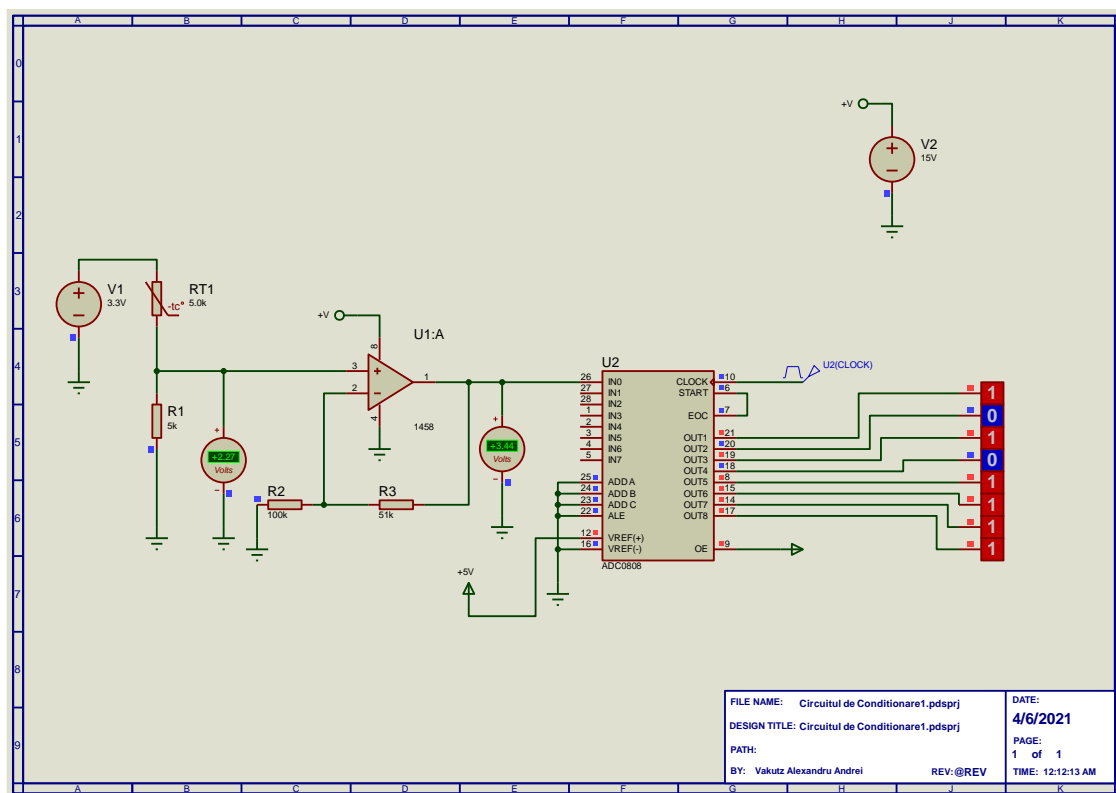


Figure 2. $R_t@45^{\circ}\text{C}$

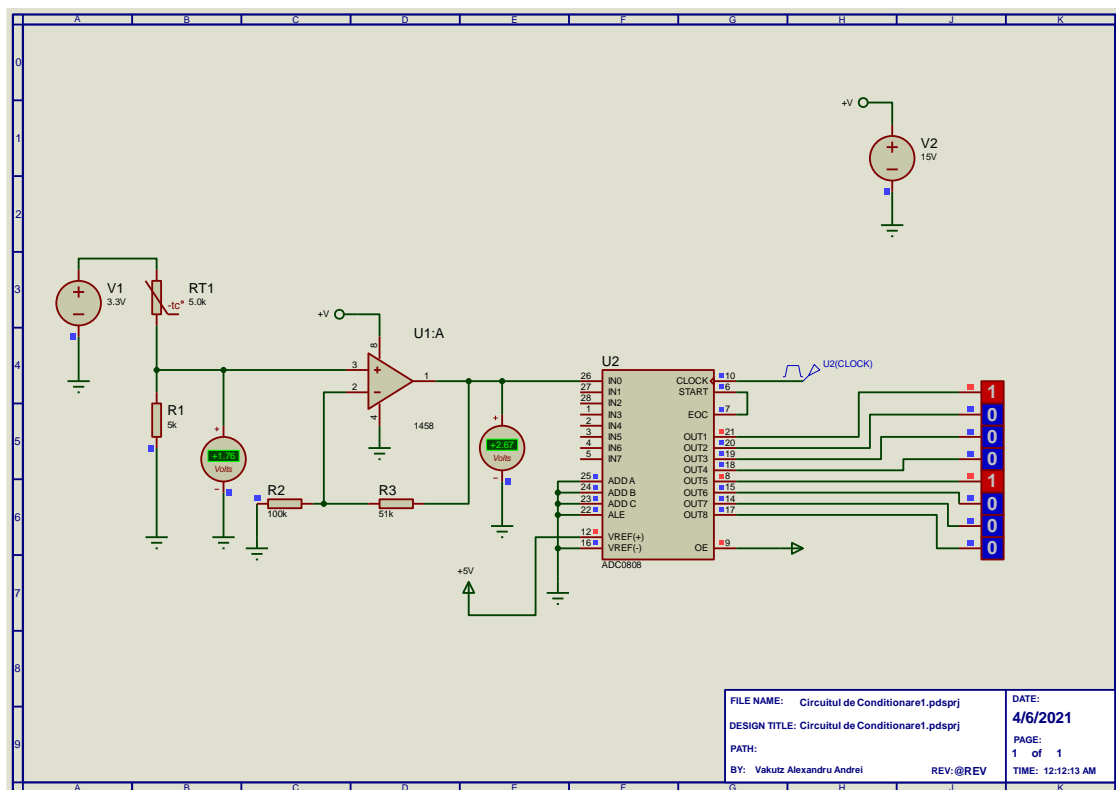


Figure 3. $R_t@28^{\circ}\text{C}$

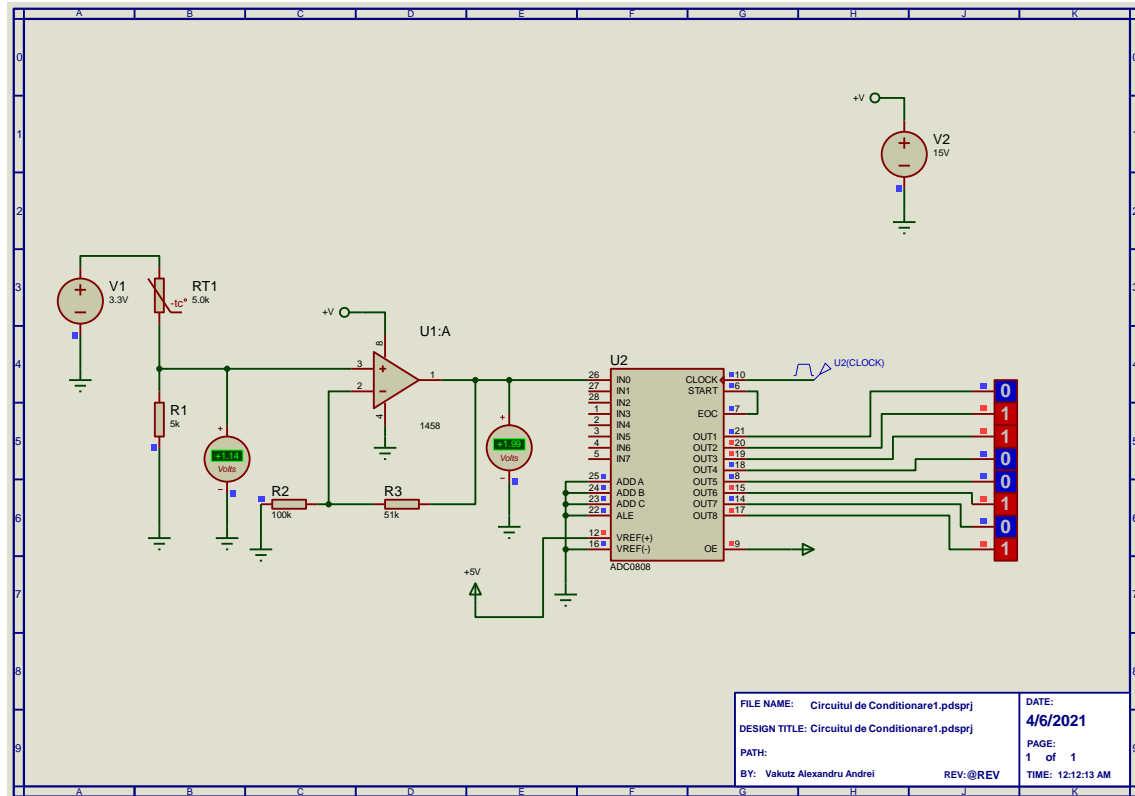


Figure 4. $R_t@10^{\circ}\text{C}$